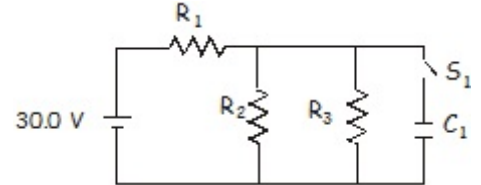


Name: _____

1. Three resistors are arranged in a circuit as shown. There is also a switch and a capacitor. R_1 is 25.0Ω , R_2 is 25.0Ω , R_3 is 45.0Ω , and C_1 has the value of $1.25 \mu\text{F}$. (a) When S_1 is open, what is the total current? (b) What is the voltage drop for R_1 ? (c) Switch S_1 is now closed for a long time. What is the charge Q on the capacitor? (d) What is the potential energy stored in the capacitor?



a. $R_{23} = (R_2^{-1} + R_3^{-1})^{-1}$
 $= ((25.0 \Omega)^{-1} + (45.0 \Omega)^{-1})^{-1} = 16.0714286 \Omega$

$R_{\text{tot}} = R_1 + R_{23}$
 $= 25.0 \Omega + 16.0714286 \Omega = 41.0714286 \Omega$

$I_{\text{tot}} = V/R_{\text{tot}}$
 $= 30.0 \text{ V}/41.0714286 \Omega = 0.73043478 \text{ A} = \boxed{0.730 \text{ A or } 730 \text{ mA}}$


b. $V_1 = R_1 I_{\text{tot}} = 25.0 \Omega \cdot 0.73043478 \text{ A} = 18.26087 \text{ V} = \boxed{18.3 \text{ V}}$

c. $V_C = V_{23} = 30.0 \text{ V} - 18.26087 \text{ V} = 11.73913 \text{ V}$
 $Q = CV = 1.25 \times 10^{-6} \text{ F} \cdot 11.73913 \text{ V} = 1.46739125 \times 10^{-5} \text{ C} = \boxed{1.47 \times 10^{-5} \text{ C or } 14.7 \mu\text{C}}$


d. $U_C = \frac{1}{2} QV = 0.5 \cdot 1.46739125 \times 10^{-5} \text{ C} \cdot 11.73913 \text{ V} = 8.612948322 \times 10^{-5} \text{ J} = \boxed{8.61 \times 10^{-5} \text{ J}}$

2. You are given a 12.0 V battery, and four resistors with the following values: 100.0Ω , 30.0Ω , 20.0Ω , and 10.0Ω . You also have plenty of wire that has essentially zero resistance. (a) Draw a circuit in which each resistor has current flowing through it, but in which the current from the battery is as small as possible. (b) Now draw a circuit in which the current from the battery is as large as possible. (no short circuiting of the battery, however.)

a.

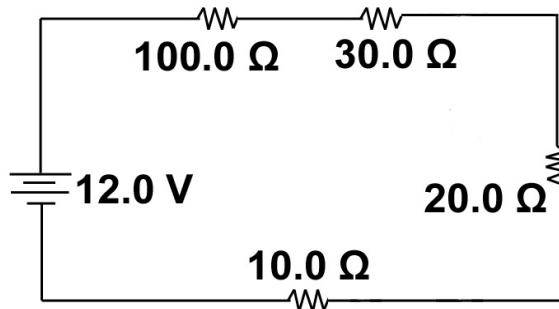

b.

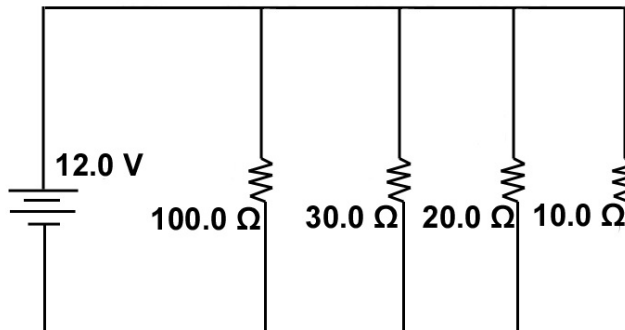

3. Find the: (a) total current, (b) total resistance, (c) power dissipated by R_4 .

a. R_1 is parallel with R_2 . R_3 is parallel with R_4 .

$$R_{12} = (R_1^{-1} + R_2^{-1})^{-1} = 306.504065 \Omega$$

$$R_{34} = (R_3^{-1} + R_4^{-1})^{-1} = 311.9521912 \Omega$$

$$R_{\text{tot}} = R_{12} + R_{34} + R_5 = 968.4562562 \Omega$$

$$I = V/R = 25 \text{ V}/968.4562562 \Omega$$

$$= 0.025814279 \text{ A} = \boxed{0.026 \text{ A or } 26 \text{ mA}}$$

b. $R_{\text{tot}} = \boxed{970 \Omega}$

c. $V_4 = I \cdot R_{34} = 0.025814279 \text{ A} \cdot 311.9521912 \Omega$


$$= 8.052820899 \text{ V}$$

or $V_4 = V_{\text{tot}} \cdot (R_{34} / R_{\text{tot}})$

$$= 25 \text{ V} \cdot (311.9521912 \Omega / 968.4562562 \Omega)$$

$$= 8.052820899 \text{ V}$$
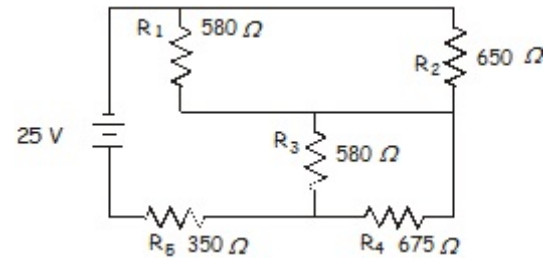
$$P = V^2/R = (8.052820899 \text{ V})^2 / 675 \Omega = 0.096070999 \text{ W} = \boxed{0.096 \text{ W or } 96 \text{ mW}}$$



4. A proton has a velocity of $1.25 \times 10^6 \text{ m/s}$. It travels into a magnetic field that has a strength of 1.50 T . What is the maximum force that the proton can experience?

$$F_b = qvB\sin\theta = 1.6 \times 10^{-19} \text{ C} \cdot 1.25 \times 10^6 \text{ m/s} \cdot 1.50 \text{ T} = \boxed{3.00 \times 10^{-13} \text{ N or } 300. \text{ fN}}$$

5. A circuit is as shown. Find: (a) the total resistance, (b) the total current, (c) the voltage provided by the battery, and (d) the amount of energy that the battery puts out in 1.00 hours in kWh.

$$\begin{aligned} \text{a. } R_T &= R_1 + (R_3^{-1} + (R_2 + (R_4^{-1} + R_5^{-1})^{-1})^{-1})^{-1} + R_6 \\ &= 47.31012658 \, \Omega = \boxed{47.3 \, \Omega} \end{aligned}$$

or (in steps):

$$R_{245} = R_2 + (R_4^{-1} + R_5^{-1})^{-1} = 14.25925926 \, \Omega$$

$$R_{2345} = (R_3^{-1} + R_{245}^{-1})^{-1} = 7.310126582 \, \Omega$$

$$R_T = R_1 + R_{2345} + R_6 = 47.310126582 \, \Omega$$

$$\text{b. } V_{245} = V_3 = R_3 \cdot I_3 = 15.0 \, \Omega \cdot 0.165 \, \text{A} = 2.475 \, \text{V}$$


$$I_T = I_3 + I_{245} = I_3 + V_{245}/R_{245} = 0.165 \, \text{A} + 2.475 \, \text{V}/14.25925926 \, \Omega$$

$$= 0.3385714286 \, \text{A} = \boxed{0.339 \, \text{A} \text{ or } 339 \, \text{mA}}$$

$$\text{c. } V_{\text{BAT}} = V_1 + V_3 + V_6 = R_1 I_T + V_3 + R_6 I_T$$

$$= 15.0 \, \Omega \cdot 0.339 \, \text{A} + 2.475 \, \text{V} + 25.0 \, \Omega \cdot 0.339 \, \text{A} = 16.01785714 \, \text{V} = \boxed{16.0 \, \text{V}}$$
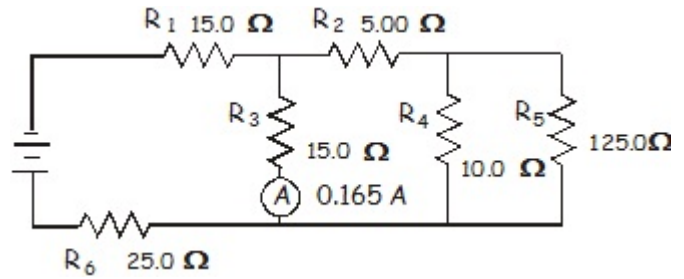
$$\text{d. } E = P \cdot t = (VI) \cdot t = 16.0 \, \text{V} \cdot 0.339 \, \text{A} \cdot 1.00 \, \text{h} = \boxed{5.424 \, \text{Wh} \text{ or } 0.005424 \, \text{kWh}}$$



6. A circuit is arranged as shown. The battery has an internal resistance of $2.5 \, \Omega$, the source of emf is $15 \, \text{V}$. Find: (a) the total current in the circuit, and (b) The voltage provided by the battery.

$$\text{a. } R_T = (25^{-1} + 85^{-1})^{-1} \, \Omega = 19.31818182 \, \Omega$$

$$I_T = V/(R_T + R_{\text{BAT}}) = 15 \, \text{V}/21.81818182 \, \Omega$$

$$= 0.6875 \, \text{A} = \boxed{0.69 \, \text{A} \text{ or } 690 \, \text{mA}}$$

$$\text{b) } V_{\text{BAT}} = V_{\text{EMF}} - R_{\text{BAT}} \cdot I = 15 \, \text{V} - 2.5 \, \Omega \cdot 0.6875 \, \text{A}$$

$$= 13.28125 \, \text{V} = \boxed{13.3 \, \text{V}}$$

